

Student Name: İrem Zeynep Alagöz

Student ID: 2018400063

Session: 1

## CMPE 240 2020 Experiment 5 Preliminary Work

### 1. State Register Inputs:

$$n1 = (x.s0'.s1') + (s0.s1)$$

$$n0 = (x'.s1) + (x.s0)$$

rst, clk

### 2. State Register Outputs:

s1,s0

### 3. Combinational Block Inputs:

x, s1,s0

### 4. Combinational Block Output:

$$y1 = s1.x'$$

$$y0 = (x'.s0'.s1') + (x.s0.s1')$$

$$n1 = (x.s0'.s1') + (s0.s1)$$

$$n0 = (x'.s1) + (x.s0)$$

### 5. Fill the following truth table:

#	s1	s0	x	n1	n0	y1	y0
0	0	0	0	0	0	0	1
1	0	0	1	1	0	0	0
2	0	1	0	0	0	0	0
3	0	1	1	0	1	0	1
4	1	0	0	0	1	1	0
5	1	0	1	0	0	0	0
6	1	1	0	1	1	1	0
7	1	1	1	1	1	0	0

Student Name: İrem Zeynep Alagöz


Student ID: 2018400063

Session: 1

6. Is this a Moore or Mealy Machine? (No explanation, only short answer)

**Mealy Machine.**

7. Draw the FSM:

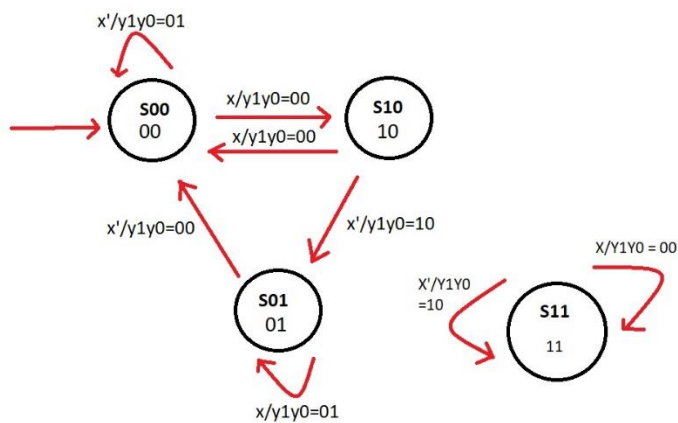


8. How many unreachable states does the finite state machine contain?

**One state. (s11)**

9. Minimize the state machine. Show your steps. Is it minimized or not?

**STEP1:**

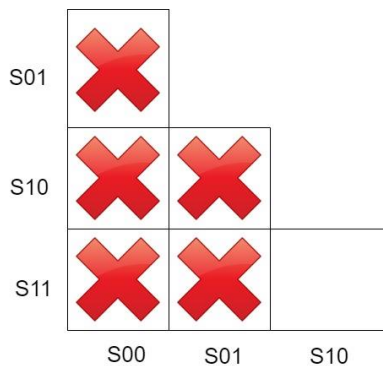






State pairs having different outputs are different, mark them. Only s10 and s11 states gives same outputs respect to same inputs.

Student Name: İrem Zeynep Alagöz

Student ID: 2018400063







Session: 1

**STEP2:**

S01			
S10			
S11			(S11, S01) (S11, S00)
	S00	S01	S10

For unmarked state write next state pairs for same input values.

**STEP3:**

S01			
S10			
S11			
	S00	S01	S10

For unmark state pairs, mark having nonequivalent next state pairs. Since (S11, S01) pair and (S11, S00) pairs are already marked as nonequivalent, mark (s11, s10) pair.

**STEP4:** There is no remaining states, so this FSM is **not minimized**.